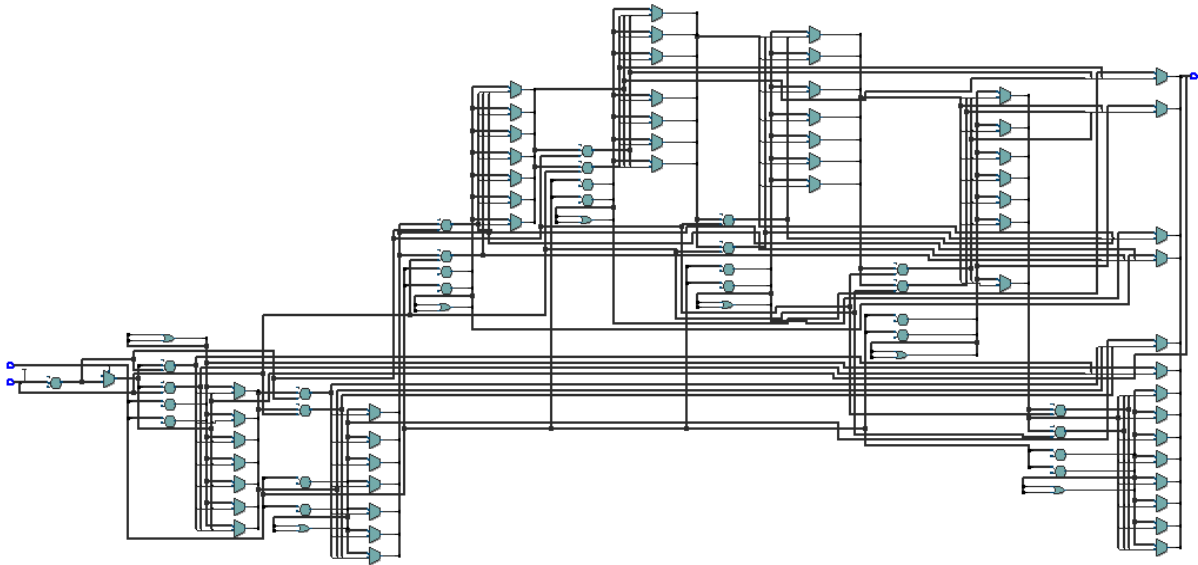


## 5. 8-bits Booth Multiplier Circuit

### Design:



- ❖ Designed a “booth\_mult” module that implements an 8×8 signed Booth multiplication also using a combinational loop to simulate arithmetic shifts.
- ❖ Actually, the multiplier design is entirely combinational logic (without FSM) having no clock signal.
- ❖ First, It initializes partial products and conditionally adds or subtracts based on the multiplier bits using Booth’s encoding.
- ❖ Finally, the result is extracted from the shifted partial product and assigned to the 16-bit output.

### Verificiation:

Wave - Default										
100 ps										
Search:										
Msgs										
/booth_mult_tb/mul...	100	127	0	-128	64	5	100			
/booth_mult_tb/mul...	1	-1	85	1	2	5	1			
/booth_mult_tb/pro...	100	-127	0	128		25	100			

```

# Applying 6 essential test cases to Booth multiplier
# multiplicand = 127, multiplier = -1, product = -127, expected = -127
# PASS
# multiplicand = 0, multiplier = 85, product = 0, expected = 0
# PASS
# multiplicand = -128, multiplier = 1, product = 128, expected = -128
# FAIL
# multiplicand = 64, multiplier = 2, product = 128, expected = 128
# PASS
# multiplicand = 5, multiplier = 5, product = 25, expected = 25
# PASS
# multiplicand = 100, multiplier = 1, product = 100, expected = 100
# PASS

```

- ❖ Designed the testbench that verified the 'booth\_mult' module by applying six signed input combinations to test essential case scenarios.
- ❖ Inside the test, there is a custom checker function block to compare the module's output against the expected result from built-in multiplication operation (\*).
- ❖ Each case is delayed and checked sequentially, with pass/fail feedback message printed for validation for result.